

Aufgabe 1

$$a) \underline{z}_{11} = \frac{U_1}{I_1} = j\omega L_1 + j\omega L_3$$

$$\underline{z}_{21} = \frac{U_2}{I_1} = j\omega L_3 + j\omega L_2$$

$$\underline{z}_{12} = \frac{U_1}{I_2} = j\omega L_3$$

$$\underline{z}_{22} = \frac{U_2}{I_2} = j\omega L_2 + j\omega L_3$$

$$\underline{z} = \begin{pmatrix} j(\omega L_1 + \omega L_3) & j\omega L_3 \\ j\omega L_3 & j(\omega L_2 + \omega L_3) \end{pmatrix}$$

$$b) \det \underline{z} = j^2 (\omega^2 L_1 L_2 + \omega^2 L_1 L_3 + \omega^2 L_2 L_3 + \omega^4 L_3^2) - j^2 \omega^4 L_3^2 \\ = -1(\dots)$$

$$\underline{Y} = \begin{pmatrix} \frac{\underline{z}_{22}}{\det \underline{z}} & \frac{-\underline{z}_{12}}{\det \underline{z}} \\ \frac{-\underline{z}_{21}}{\det \underline{z}} & \frac{\underline{z}_{11}}{\det \underline{z}} \end{pmatrix} = \begin{pmatrix} \frac{j\omega(L_1 + L_2)}{j\omega^2(L_1 L_2 + L_1 L_3 + L_2 L_3 + L_3^2)} & \frac{-j\omega L_3}{j\omega^4 \dots} \\ \frac{-L_3}{j\omega(L_1 L_2 + L_1 L_3 + L_2 L_3 + L_3^2)} & \frac{L_2 + L_3}{j\omega(L_1 L_2 + L_1 L_3 + L_2 L_3 + L_3^2)} \end{pmatrix}$$

$$c) \underline{Y} = \begin{pmatrix} \frac{1}{R_1} + \frac{1}{R_2} & -\frac{1}{R_2} \\ -\frac{1}{R_2} & \frac{1}{R_2} + \frac{1}{R_3} \end{pmatrix}$$

$$\underline{Y}_{11} = \frac{I_1}{U_1} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\underline{Y}_{12} = \frac{I_1}{U_2} = -\frac{1}{R_2}$$

$$\underline{Y}_{21} = \frac{I_2}{U_1} = -\frac{1}{R_2}$$

$$\underline{Y}_{22} = \frac{I_2}{U_2} = \frac{1}{R_2} + \frac{1}{R_3}$$

$$\det \underline{Y} = \left(\frac{1}{R_1} + \frac{1}{R_2}\right) \left(\frac{1}{R_2} + \frac{1}{R_3}\right) - \frac{1}{R_2^2}$$

$$= \frac{1}{R_1 R_2} + \frac{1}{R_1 R_3} + \frac{1}{R_2^2} + \frac{1}{R_2 R_3} - \frac{1}{R_2^2}$$

$$= \frac{1}{R_1 R_2} + \frac{1}{R_1 R_3} + \frac{1}{R_2 R_3} = \frac{R_1 + R_2 + R_3}{R_1 R_2 R_3}$$



$$\underline{Z} = \frac{\left(\frac{1}{R_2} + \frac{1}{R_3}\right) (R_1 R_2 R_3)}{R_1 + R_2 + R_3}$$

$$\underline{Z} = \begin{pmatrix} \frac{R_1 R_2 + R_1 R_3}{R_1 + R_2 + R_3} & \frac{R_1 R_3}{R_1 + R_2 + R_3} \\ \frac{R_1 R_3}{R_1 + R_2 + R_3} & \frac{R_2 R_3 + R_1 R_3}{R_1 + R_2 + R_3} \end{pmatrix}$$

$$f) \underline{Z}_2 = \underline{Z}_1 + \underline{Z}_2 = \begin{pmatrix} \frac{R_1 R_2 + R_1 R_3}{R_1 + R_2 + R_3} + j\omega(L_1 + L_2) & \frac{R_1 R_3}{R_1 + R_2 + R_3} + j\omega L_3 \\ \frac{R_1 R_3}{R_1 + R_2 + R_3} + j\omega L_3 & \frac{R_2 R_3 + R_1 R_3}{R_1 + R_2 + R_3} + j\omega(L_2 + L_3) \end{pmatrix}$$

$$e) \underline{Y} = \underline{Y}_1 + \underline{Y}_2 = \begin{pmatrix} \frac{L_1 + L_2}{j\omega(L_1 L_2 + L_1 L_3 + L_2 L_3)} + \frac{1}{R_1} + \frac{1}{R_2} & -\frac{L_3}{j\omega(L_1 L_2 + L_1 L_3 + L_2 L_3)} - \frac{1}{R_2} \\ -\frac{L_3}{j\omega(L_1 L_2 + L_1 L_3 + L_2 L_3)} - \frac{1}{R_2} & \frac{L_2 + L_3}{j\omega(L_1 L_2 + L_1 L_3 + L_2 L_3)} + \frac{1}{R_2} + \frac{1}{R_3} \end{pmatrix}$$

Aufgabe 2

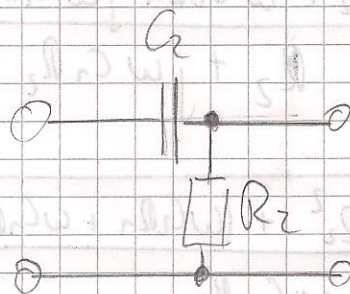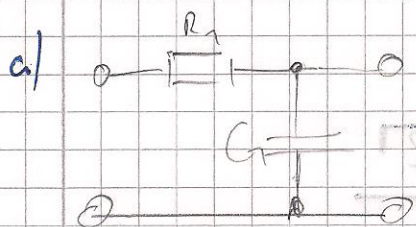

$$b) \underline{z}_{-11} = \frac{u_1}{I_2} = R_1 + j\omega C_1$$

$$\underline{z}_{-11} = R_2 + j\omega C_2$$

$$\underline{z}_{-21} = \frac{u_2}{I_1} = j\omega C_1$$

$$\underline{z}_{-21} = \frac{u_2}{I_1} = R_2$$

$$\underline{z}_{-12} = j\omega C_1$$

$$\underline{z}_{-12} = R_2$$

$$\underline{z}_{-22} = j\omega C_1$$

$$\underline{z}_{-22} = R_2$$

$$[\underline{z}_{-1}] = \begin{pmatrix} R_1 + j\omega C_1 & j\omega C_1 \\ j\omega C_1 & j\omega C_1 \end{pmatrix}$$

$$[\underline{z}_{-2}] = \begin{pmatrix} R_2 + j\omega C_2 & R_2 \\ R_2 & R_2 \end{pmatrix}$$

$$\det \underline{z} = j\omega C_1 R_1 - \omega^2 C_1^2 + \omega^2 C_1^2 = j\omega C_1 R_1$$

$$\det \underline{z} = R_2^2 + j\omega C_2 R_2 - R_2^2 = j\omega C_2 R_2$$

$$[\underline{A}_1] = \begin{pmatrix} \frac{R_1 + j\omega C_1}{j\omega C_1} & R_1 \\ 1 & 1 \end{pmatrix} \begin{pmatrix} \frac{R_2 + j\omega C_2}{R_2} & \frac{j\omega C_2 R_2}{R_2} \\ \frac{1}{R_2} & 1 \end{pmatrix} = [\underline{A}_c]$$

$$A_{11, \text{kompl. Schr.}} = \frac{u_2}{u_1} = \frac{R_1 + j\omega C_1}{j\omega C_1} \cdot \frac{R_2 + j\omega C_2}{R_2} + \frac{R_1}{j\omega C_1 \cdot R_2} = H(f)$$

$$H(f) = \frac{R_1 R_2 + R_1 j\omega C_2 + R_2 j\omega C_1 + \omega^2 C_1 C_2}{R_2 j\omega C_1} + \frac{R_1}{R_2}$$

$$H(f) = \frac{R_1 R_2 + j\omega C_1 R_1 + j\omega C_1 R_2 + R_1 j\omega C_1}{j\omega C_1 R_2}$$

$$|H(f)| = \frac{\sqrt{R_1 R_2^2 + (\omega C_1 R_1 + \omega C_1 R_2 + \omega R_1 C_1)^2}}{\omega C_1 R_2}$$